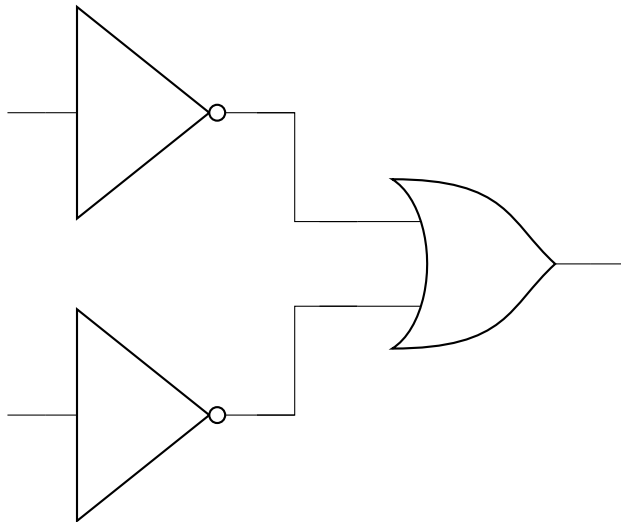


Assignment

January 9, 2024

Gate question

1. The above combination of logic gate represent the operation



- (a) OR
- (b) NAND
- (c) AND
- (d) NOR

(GATE PH 2021)